

secondary reverse, allowing diodes D3 and D4 to conduct. The energy stored in the transformer during the on-time is transferred to the output during the transistor off-time.

The MIC6211 op amp, U2, is needed to invert and attenuate the negative output voltage before it can be connected to the feedback pin of U1. Resistors R4 and R5 serve a dual purpose. They are part of the output voltage setting network and provide a minimum load to the -70V output. Two resistors (R4 and R5) share the power dissipation. Resistors R3, R4 and R5 set the output voltage according to the formula below.

$$(1) \quad V_{\text{OUT}} = -1.24V \left(\frac{R4 + R5}{R3} \right)$$

The power dissipated in resistor R4 or R5 is calculated in Equation 2.

$$(2) \quad P_{\text{DISS}} = \frac{\left(\frac{1}{2} V_{\text{OUT}} \right)^2}{R4}$$

For the evaluation circuit R4 and R5 each dissipate 90mW. Zener diode D6 increases the input undervoltage lockout threshold of the MIC2171. The turn on threshold of the MIC2171 is typically 2.7V at 25°C. The 3.9V Zener will prevent the IC from starting up until the input voltage reaches a minimum of 6.7V. Diode D2 is used to prevent the -24V output from temporarily going positive when the -70V output is short-circuited. The diode protects the tantalum capacitors from reverse voltage damage.

Referencing Figure 1, there are three secondary windings, each having an equal number of turns. The sum of the three windings plus two diode drops is equal to the regulated output voltage of -70V (ignoring resistive losses). Therefore, 23.7V is developed across each winding, assuming a 0.6V diode drop. The output voltage on the -24V section is closer to -23.1V. The -70V output is achieved by stacking a -47V section (two windings in series) on top of the -24V output.

This technique improves the cross regulation over using individual -24V and -70V output sections. Other advantages of this technique are lower voltage stresses on the output capacitors and fewer windings on the power transformer.

The coupling between the primary and secondary is not ideal and therefore, not all of the energy stored in the inductor is transferred to the secondary. This non-ideal coupling appears as a leakage inductance, which forces current to flow in the primary for a short time after the transistor turns off. Diodes D1 and D5 form a clamping circuit which provides a path for this leakage current to flow and limits the maximum voltage on the switching transistor to 24V. The clamp voltage must be greater than the maximum flyback voltage, which appears across the primary winding during the "off time". The flyback voltage across the primary winding is equal to the voltage across the secondary winding times the transformer turns ratio.

$$V_{\text{flyback}} = V_{\text{secondary}} \left(\frac{N_{\text{primary}}}{N_{\text{secondary}}} \right) = 23.3V \frac{1}{2.93}$$

$$V_{\text{flyback}} = 8V$$

The peak primary current is calculated from Equation 3.

$$(3) \quad I_P = \sqrt{\frac{2P_{\text{OUT}} t}{\eta L_{\text{PRI}}}}$$


$$I_P = \sqrt{\frac{2 \times 5.5W \times 10\mu s}{0.75 \times 30\mu H}}$$

$$I_P = 2.21A$$


Parts List

Reference	Vendor	Part Number	Description	Quantity
U1	Micrel	MIC2171BU	100kHz switching regulator	1
U2	Micrel	MIC6211BM5	IttyBitty™ operational amplifier	1
C1, C2-4, C7	AVX	TPSE226M035R0300	22μF, 35V, tant.	5
C5	AVX	12063C224MATMA	0.22μF, ceramic	1
C6	AVX	08055C103MATMA	0.01μF, ceramic	1
C8	AVX	08055C332MATMA	3300pF, ceramic	1
C9	AVX	08055C221MATMA	220pF, ceramic	1
D1, D3, D4	Motorola	MURS120T3	1A, 200V ultrafast	3
D2	G.I.	RS1B	1A, 100V diode	1
D5	G.I.	SMAJ22A	22V TVS	1
D6	Motorola	MMB25228BLT1	3.9V Zener, 1/4W	1
R1		0805-size resistor	3.32k 1% metal film	1
R2		0805-size resistor	10k 1% metal film	1
R3		0805-size resistor	487Ω 1% metal film	1
R4		1206-size resistor	13.7k 1% metal film	1
R5		1206-size resistor	13.7k 1% metal film	1
T1	Beckman	HM00-98519	flyback transformer	1


PCB Layouts

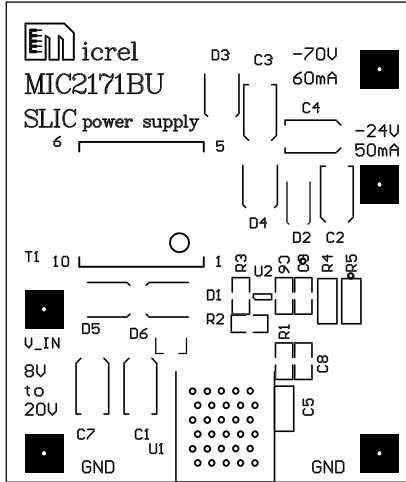


Component-Side Silk Screen

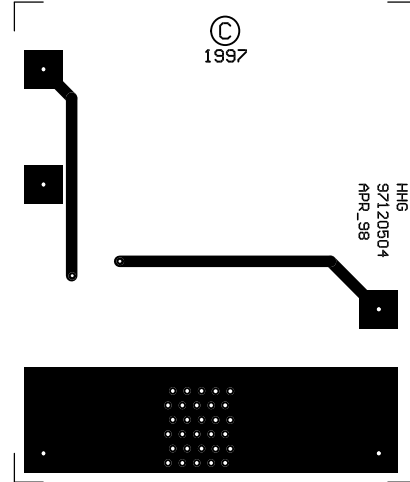

Solder-Side Copper

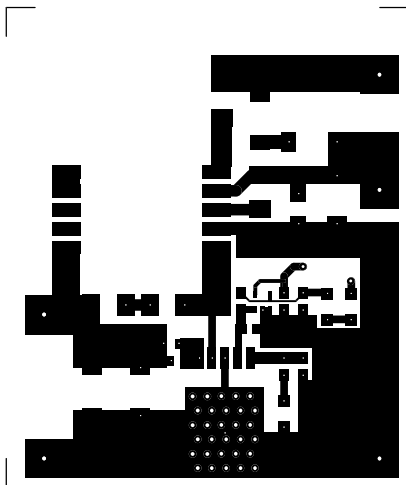

Component-Side Copper

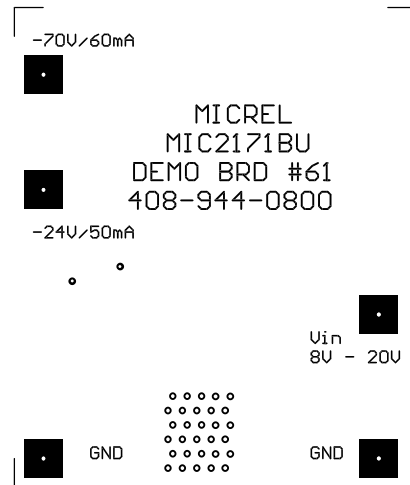

Solder-Side Silk Screen

MICREL INC. 1849 FORTUNE DRIVE SAN JOSE, CA 95131 USA

TEL + 1 (408) 944-0800 FAX + 1 (408) 944-0970 WEB <http://www.micrel.com>

This information is believed to be accurate and reliable, however no responsibility is assumed by Micrel for its use nor for any infringement of patents or other rights of third parties resulting from its use. No license is granted by implication or otherwise under any patent or patent right of Micrel Inc.

© 1998 Micrel Incorporated